

**Assignment Solutions**

1. Design an ALU with 3 inputs i.e two 16-bit signed values and a 4-bit control signal which perform ALU Operation? The ALU has 16 bit signed output?

Control Signal	ALU Operation
0000	Out = A xor b
0001	Out = A and b
0010	Out = A or B
0011	Out = A xnor B
0100	Out = A nand B
0101	Out = A nor B
0110	Out = A + B
0111	Out = A - B
1000	Out = A*B
1001	Out = A/B
1010	Out = A << 1
1011	Out = A >> 1
1100	Out = A/B rotated left by 1
1101	Out = A/B rotated right by 1
1110	Out = A > B
1111	Out = A < B

## **Source Code**

```
`timescale 1ns / 1ps

module alu( a,b,ctrl,out );

input signed [15:0]a,b;
input [3:0]ctrl;

output reg signed [15:0]out;

always@(*)

begin

    case(ctrl)
        0:out=a^b;
        1:out=a&b;
        2:out=a|b;
        3:out= (a^^b) ;
        4:out= ~(a&b);
        5:out= ~(a|b);
        6:out=a+b;
        7:out=a-b;
        8:out=a*b;
        9:out=a/b;
        10:out=a<<1;
        11:out=a>>1;
        12:out=(a/b)<<1;
        13:out=(a/b)>>1;
        14:out=a>b;
        15:out=a<b;

        default: $display("_Invalid_");

    endcase
end

endmodule
```

# **Test Bench Code**

```
`timescale 1ns / 1ps

module tb_alu;

    // Inputs
    reg [15:0] a;
    reg [15:0] b;
    reg [3:0] ctrl;

    // Outputs
    wire [15:0] out;

    // Instantiate the Unit Under Test (UUT)


    alu uut (
        .a(a),
        .b(b),
        .ctrl(ctrl),
        .out(out)
    );

    initial begin
        // Initialize Inputs
        a = 3;
        b = 2;
        ctrl = 0;
        ctrl = 0; #160;
        $stop;
    end


    always
        #10 ctrl=ctrl+1;

Endmodule
```

**Simulation Output**

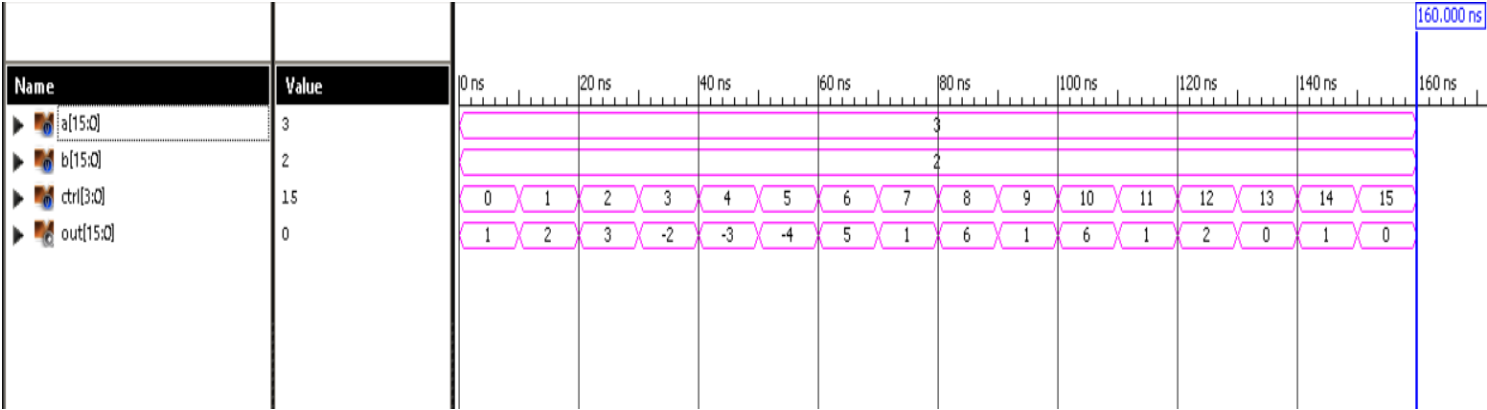

**RTL Schematic**

 

2. Simulate and implement binary “101001/101000” sequence detector for the following:

- (a) Moore FSM without sequence overlap
- (b) Moore FSM with sequence overlap
- (c) Mealy FSM without sequence overlap
- (d) Mealy FSM with sequence overlap

### **A. Moore FSM without sequence overlap**

#### **Source Code**

```
`timescale 1ns / 1ps
module moore_without (sequence_in, clock, reset, out );
input clock;
input reset;
input sequence_in;
output reg out;
parameter A=3'b000,
          B=3'b001,
          C=3'b010,
          D=3'b011,
          E=3'b100,
          F=3'b101,
          G=3'b110;
reg [2:0] current_state, next_state;

always @(posedge clock, posedge reset)
begin
    if(reset==1)
        current_state <= A;
    else
        current_state <= next_state;
end

always @(current_state,sequence_in)
begin
```

```
case(current_state)
A:begin
  if(sequence_in==1)
    next_state = B;
  else
    next_state = A;
end
```

```
B:begin
  if(sequence_in==1)
    next_state = B;
  else
    next_state = C;
end
```

```
C:begin
  if(sequence_in==1)
    next_state = D;
  else
    next_state = A;
end
```

```
D:begin
  if(sequence_in==1)
    next_state = B;
  else
    next_state = E;
end
```

```
E:begin
  if(sequence_in==1)
    next_state = D;
  else
    next_state = F;
end
```

```
F:begin
  if(sequence_in==1)
    next_state = G;
  else
    next_state = A;
end
```

```
G:begin
  if(sequence_in==1)
    next_state = B;
  else
```

```
    next_state = A;  
end
```

```
default:next_state = A;  
endcase  
end
```

```
always @(current_state)  
begin  
    case(current_state)  
        A : out = 0;  
        B : out = 0;  
        C : out = 0;  
        D : out = 0;  
        E : out = 0;  
        F : out = 0;  
        G : out = 1;  
  
        default: out = 0;  
    endcase  
end  
  
endmodule
```

## **Test Bench Code**

```
`timescale 1ns / 1ps
module tb_moore_without;

    reg sequence_in;
    reg clock;
    reg reset;
    wire out;
    moore_without uut (
        .sequence_in(sequence_in),
        .clock(clock),
        .reset(reset),
        .out(out)
    );

    initial begin

        clock = 0;
        forever #20 clock = ~clock;
    end

    initial begin

        sequence_in = 0;
        reset = 1;
        #40;

        reset = 0;
        #40;

        // 101001
        sequence_in = 1; #40;
        sequence_in = 0; #40;
        sequence_in = 1; #40;
        sequence_in = 1; #40;
        sequence_in = 1; #40;

        sequence_in = 1; #40;
        sequence_in = 0; #40;
        sequence_in = 1; #40;
        sequence_in = 0; #40;
        sequence_in = 0; #40;
        sequence_in = 1; #40; //done

        sequence_in = 1; #40;
        sequence_in = 0; #40;
        sequence_in = 1; #40;
```




```

sequence_in = 0; #40;
sequence_in = 0; #40;
sequence_in = 1; #40; //done
sequence_in = 0; #40;
sequence_in = 0; #40;


end
endmodule

```

### Simulation Output

 

### RTL Schematic

 

## **B. Moore FSM with sequence overlap**

### **Source Code**

```
`timescale 1ns / 1ps
module moore_with(sequence_in,clock,reset,out
);

input clock;
input reset;
input sequence_in;
output reg out;
parameter A=3'b000,
          B=3'b001,
          C=3'b010,
          D=3'b011,
          E=3'b100,
          F=3'b101,
          G=3'b110;

reg [2:0] current_state, next_state;

always @(posedge clock, posedge reset)
begin
    if(reset==1)
        current_state <= A;
    else
        current_state <= next_state;
end

always @(current_state,sequence_in)
begin
    case(current_state)
    A:begin
        if(sequence_in==1)
            next_state = B;
        else
            next_state = A;
    end
```

```
B:begin
  if(sequence_in==1)
    next_state = B;
  else
    next_state = C;
end
```

```
C:begin
  if(sequence_in==1)
    next_state = D;
  else
    next_state = A;
end
```

```
D:begin
  if(sequence_in==1)
    next_state = B;
  else
    next_state = E;
end
```

```
E:begin
  if(sequence_in==1)
    next_state = D;
  else
    next_state = F;
end
```

```
F:begin
  if(sequence_in==1)
    next_state = G;
  else
    next_state = A;
end
```

```
G:begin
  if(sequence_in==1)
    next_state = B;
  else
    next_state = C;
end
```

```
default:next_state = A;
endcase
end
```

```

always @(current_state)
begin
    case(current_state)
A : out = 0;
B : out = 0;
C : out = 0;
D : out = 0;
E : out = 0;
F : out = 0;
G : out = 1;

    default: out = 0;
    endcase
end

endmodule

```

## **Test Bench Code**

```

`timescale 1ns / 1ps
module tb_moore_with;
    reg sequence_in;
    reg clock;
    reg reset;
    wire out;

    moore_with uut (
        .sequence_in(sequence_in),
        .clock(clock),
        .reset(reset),
        .out(out)
    );

    initial begin
        clock = 0;
        forever #20 clock = ~clock;
    end

    initial begin

```

```
sequence_in = 0;
```

```
reset = 1;
```

```
#40;
```

```
reset = 0;
```

```
#40;
```

```
// 101001
```

```
sequence_in = 1; #40;
```

```
sequence_in = 0; #40;
```

```
sequence_in = 1; #40;
```

```
sequence_in = 0; #40;
```

```
sequence_in = 1; #40;
```

```
sequence_in = 0; #40;
```

```
sequence_in = 0; #40;
```

```
sequence_in = 1; #40; //done
```

```
sequence_in = 0; #40; // break the seq
```

```
sequence_in = 1; #40;
```

```
sequence_in = 0; #40;
```

```
sequence_in = 1; #40;
```

```
sequence_in = 0; #40;
```

```
sequence_in = 0; #40;
```

```
sequence_in = 1; #40; //done
```

```
sequence_in = 0; #40;
```

```
sequence_in = 1; #40;
```

```
sequence_in = 0; #40;
```


```
sequence_in = 0; #40;
```

```
sequence_in = 1; #40; //done
```


```
end
```

```
endmodule
```

## Simulation Output

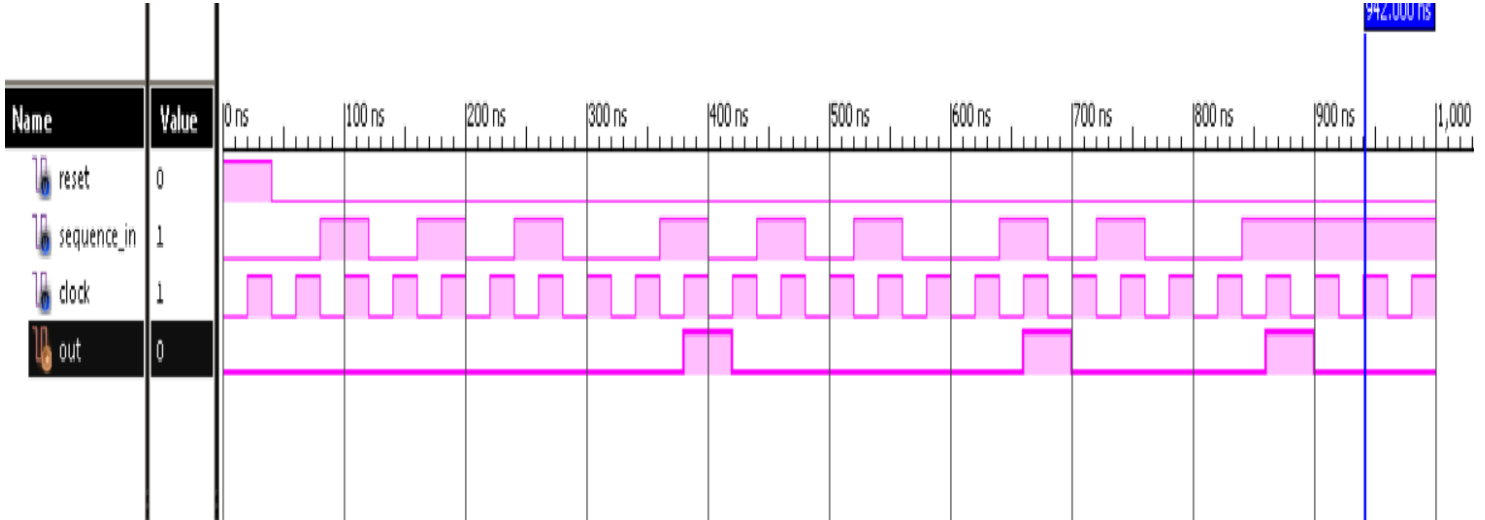

## RTL Schematic

 

## C. Mealy FSM without sequence overlap

### Source Code

```
`timescale 1ns / 1ps
module mealy_without(din, reset, clk, y);
input din;
input clk;
input reset;
output reg y;
reg [2:0] cst, nst;
parameter A = 3'b000, B = 3'b001, C = 3'b010, D = 3'b011, E = 3'b100, F = 3'b101;
always @(cst or din)
begin
case (cst)
A: if (din == 1'b1)
begin
nst = B;
y=1'b0;
end
else
begin
nst = A;
y=1'b0;
end

B: if (din == 1'b1)
begin
nst = B;
y=1'b0;
end
else
begin
nst = C;
y=1'b0;
end

C: if (din == 1'b1)
begin
nst = D;
y=1'b0;
end
else
begin
nst = A;

```

```

        y=1'b0;
    end

D: if (din == 1'b1)
    begin
        nst = B;
        y=1'b0;
    end
else
    begin
        nst = E;
        y=1'b0;
    end

E: if (din == 1'b1)
    begin
        nst = D;
        y=1'b0;
    end
else
    begin
        nst = F;
        y=1'b0;
    end

F: if (din == 1'b1)
    begin
        nst = A;
        y=1'b1;
    end
else
    begin
        nst = A;
        y=1'b0;
    end
default: nst = A;
endcase
end

always@(posedge clk)
    begin
        if (reset)
            cst <= A;
        else
            cst <= nst;
        end
endmodule

```




## **Test Bench Code**

```
`timescale 1ns / 1ps
module tb_mealy_without;
    reg din;
    reg reset;
    reg clk;
    wire y;
    mealy_without uut (
        .din(din),
        .reset(reset),
        .clk(clk),
        .y(y)
    );
    initial begin
        din = 0;
        reset = 0;
        clk = 0; #20;
        // 101001 is our sequence
        #10 din=1;
        #10 din=0;
        #10 din=1;
        #10 din=0;
        #10 din=0;
        #10 din=1; //done

        #10 din=0;
        #10 din=0;


        #10 din=1;
        #10 din=0;
        #10 din=1;
        #10 din=0;
        #10 din=0;
        #10 din=1; //done
    end
    always
        #5 clk=~clk;
endmodule
```

### Simulation Output

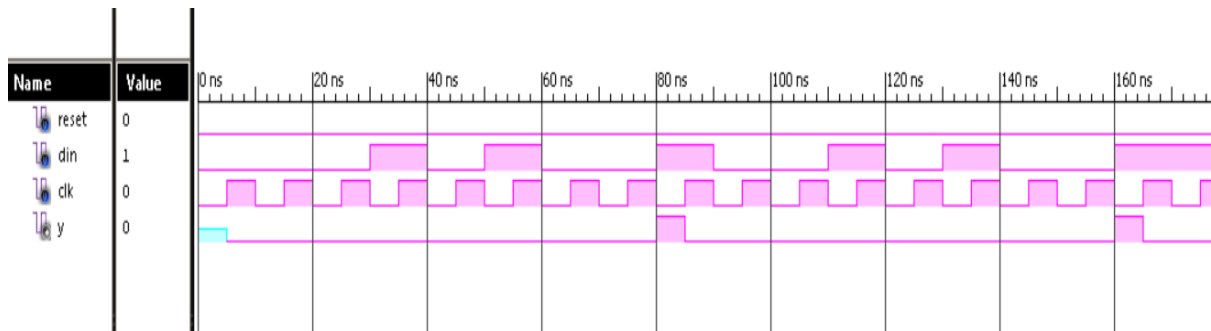

### RTL Schematic

mealy\_without

 

mealy\_without

## **D. Mealy FSM with sequence overlap**

### **Source Code**

```
`timescale 1ns / 1ps

module mealy_with(din, reset, clk, y);
input din;
input clk;
input reset;
output reg y;
reg [2:0] cst, nst;
parameter A = 3'b000,B = 3'b001,C = 3'b010,D = 3'b011, E = 3'b100,F = 3'b101;
always @(cst or din)
begin
case (cst)
A: if (din == 1'b1)
begin
nst = B;
y=1'b0;
end
else
begin
nst = A;
y=1'b0;
end

B: if (din == 1'b1)
begin
nst = B;
y=1'b0;
end
else
begin
nst = C;
y=1'b0;
end

C: if (din == 1'b1)
begin
nst = D;
y=1'b0;
end
else
begin
nst = A;

```

```
y=1'b0;  
end
```

```
D: if (din == 1'b1)  
    begin  
        nst = B;  
        y=1'b0;  
    end  
else  
    begin  
        nst = E;  
        y=1'b0;  
    end
```

```
E: if (din == 1'b1)  
    begin  
        nst = D;  
        y=1'b0;  
    end  
else  
    begin  
        nst = F;  
        y=1'b0;  
    end
```

```
F: if (din == 1'b1)  
    begin  
        nst = B;  
        y=1'b1;  
    end  
else  
    begin  
        nst = A;  
        y=1'b0;  
    end
```

```
default: nst = A;  
endcase  
end  
always@(posedge clk)  
    begin  
        if (reset)  
            cst <= A;  
        else  
            cst <= nst;  
        end  
endmodule
```

## **Test Bench Code**

```
`timescale 1ns / 1ps
module tb_mealy_with;
    reg din;
    reg reset;
    reg clk;
    wire y;
    mealy_with uut (
        .din(din),
        .reset(reset),
        .clk(clk),
        .y(y)
    );

    initial begin

        din = 0;
        reset = 0;
        clk = 0;
        #20;
        //101001
        #10 din=1;
        #10 din=0;

        #10 din=1;
        #10 din=0;
        #10 din=1;
        #10 din=0;
        #10 din=0;
        #10 din=1; //done


        #10 din=0;
        #10 din=1;
        #10 din=0;
        #10 din=0;
        #10 din=1; //done

    end

    always
        #5 clk=~clk;

endmodule
```

### Simulation Output

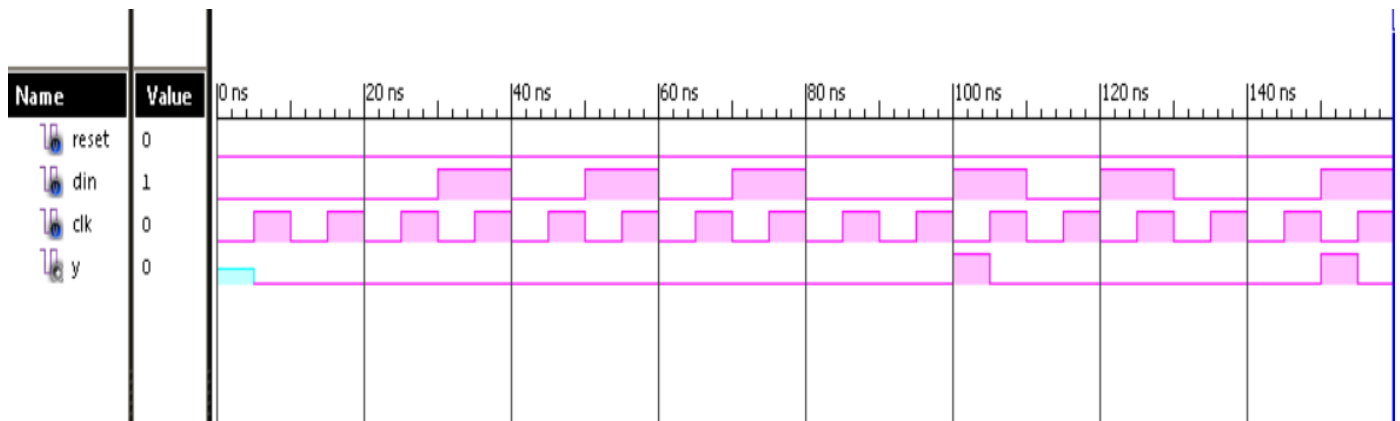

### RTL Schematic

